

Make your own!

Switches and building electrical circuits

Lesson 4: Worksheet 1



Cut out the images, and use them to build a circuit that will either light a bulb, move a motor or work a buzzer.

Wires



Bulb



Buzzer



Crocodile clips



Wires



Motor



Cell



Crocodile clips



Crocodile clips



Wires

