

How does electricity work?


Building electrical circuits

Lesson 2: Worksheet 3



Electrical symbols

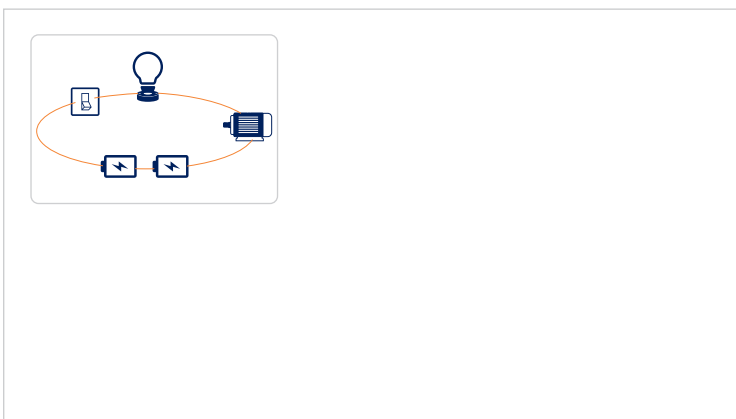Draw the circuits using the electrical symbols below



1 cell battery = 1.5V	Bulb
Bell	Connecting wire
Two 1.5V cells connected together = 3V battery	Motor

