



Conductors and insulators

Lesson 3: Worksheet 1

Cut out the below symbols, and use them to build an electrical circuit that would make the light, buzzer or motor work.



Cell



Connecting wire



Connecting wire



Motor



Bulb



Buzzer



Two cells together



Connecting wire

